

CS 311 Computer Architecture


2025/2026

Lecture 2


Assis. Prof. Dr. Elmahdy Maree

A Top-Level View of Computer Function and Interconnection

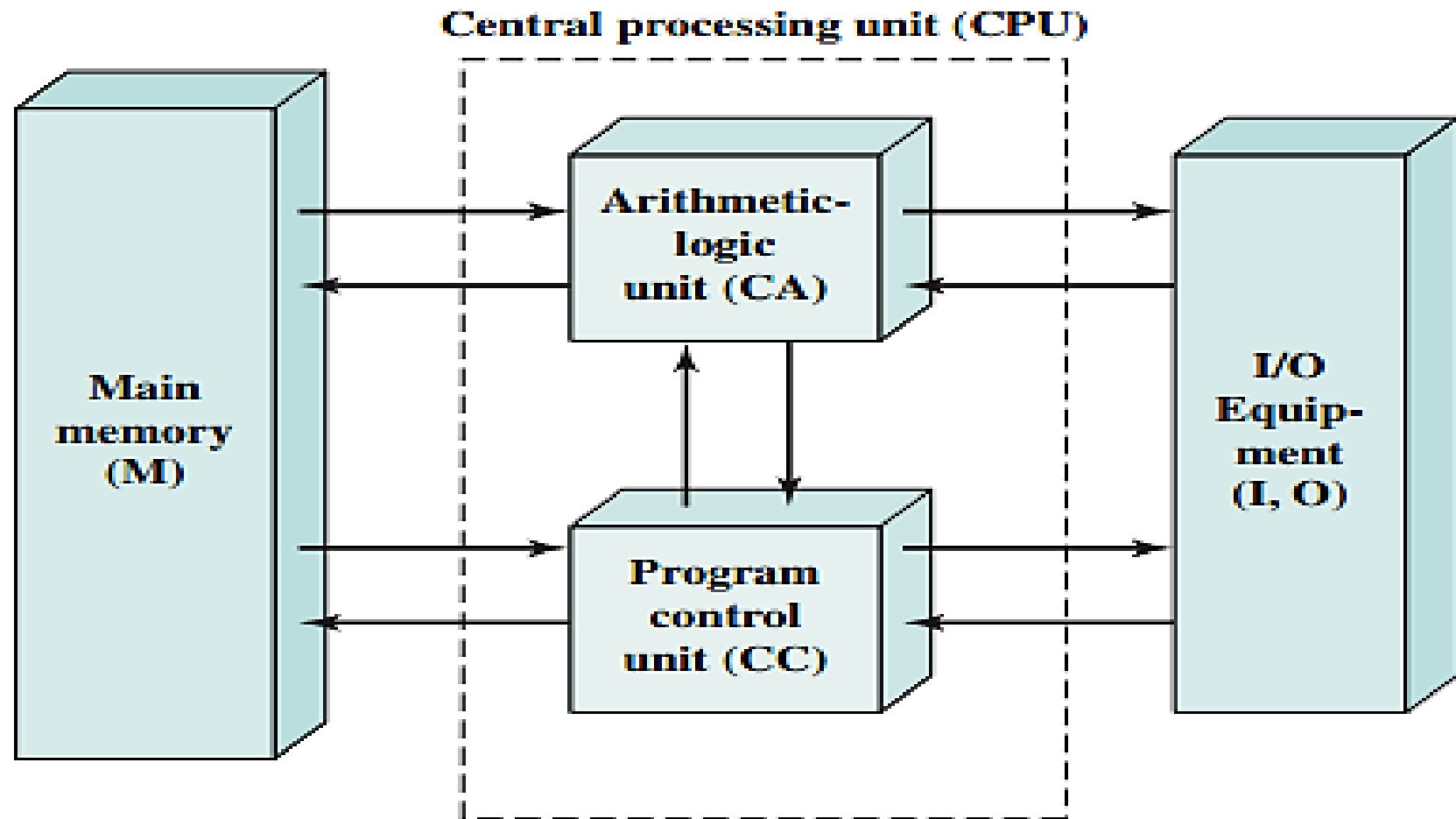A Top-Level View of Computer Interconnection



Computer Components: Top-Level View

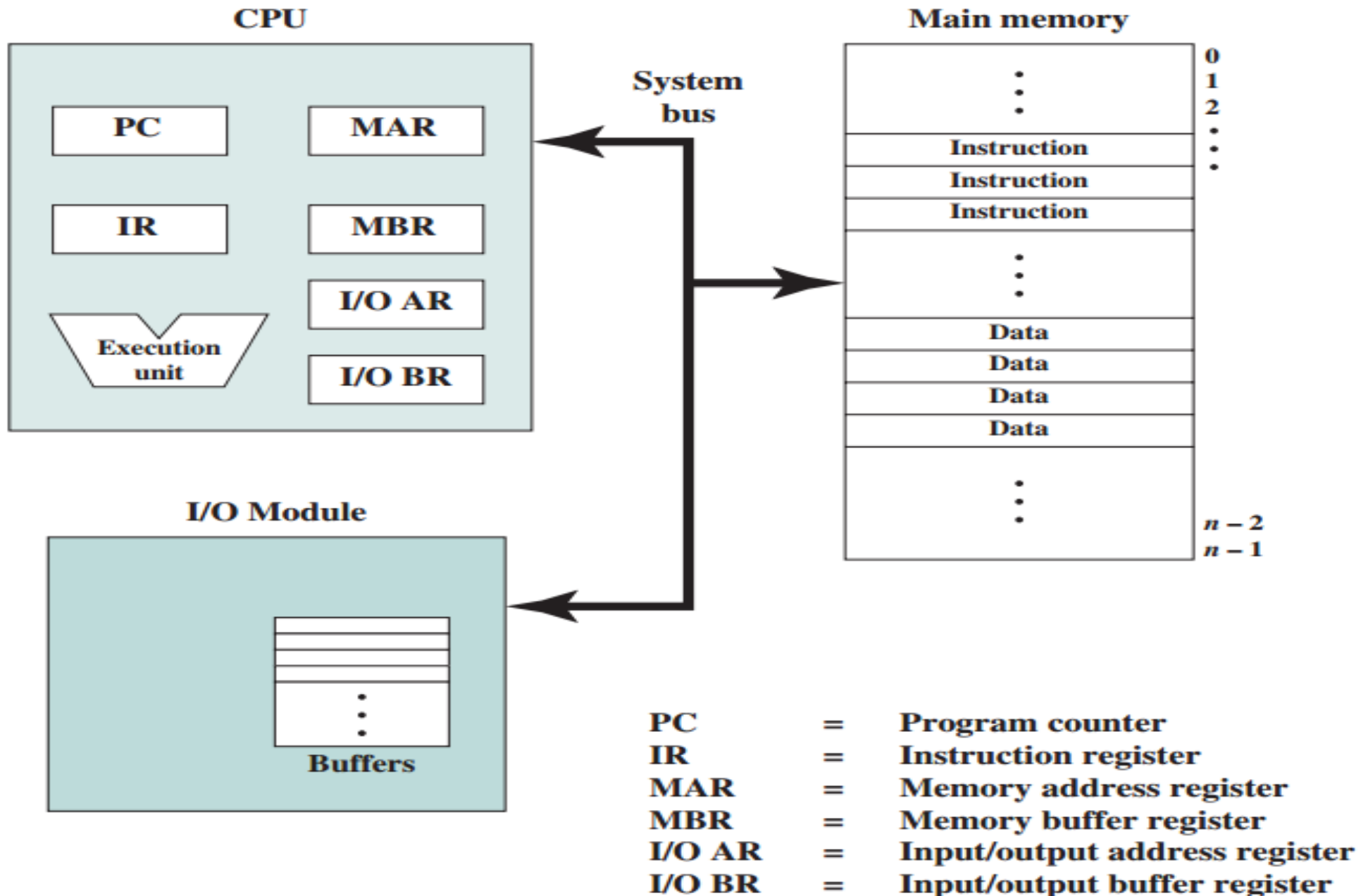

IAS stands for Princeton Institute for Advanced Studies. (Von Neumann)


Digital Building Blocks

- 1. Registers**
- 2. BUS System**
- 3. COUNTERS**
- 4. RAMS**

COUNTERS

- A. SYNCHRONOUS COUNTERS**
- B. ASYNCHRONOUS (RIPPLE) COUNTERS**

SYNCHRONOUS COUNTERS

 

CH 1: Digital Building Blocks (Registers, Counters,..)


Design of Sequential Circuit

Example 1:

Design a 3 bit Counter (Using “T” FF) which counts in binary form as follows;
000, 001, 010, ... 111, 000, 001, ...

Solution


2- State diagram:

 

Lecture 2: Sequential Circuit

CH 1: Digital Building Blocks (Registers, Counters,.)


4- State Table:

 

Lecture 2: Sequential Circuit

CH 1: Digital Building Blocks (Registers, Counters,.)


5- K-Map for FFs inputs and circuit Outputs

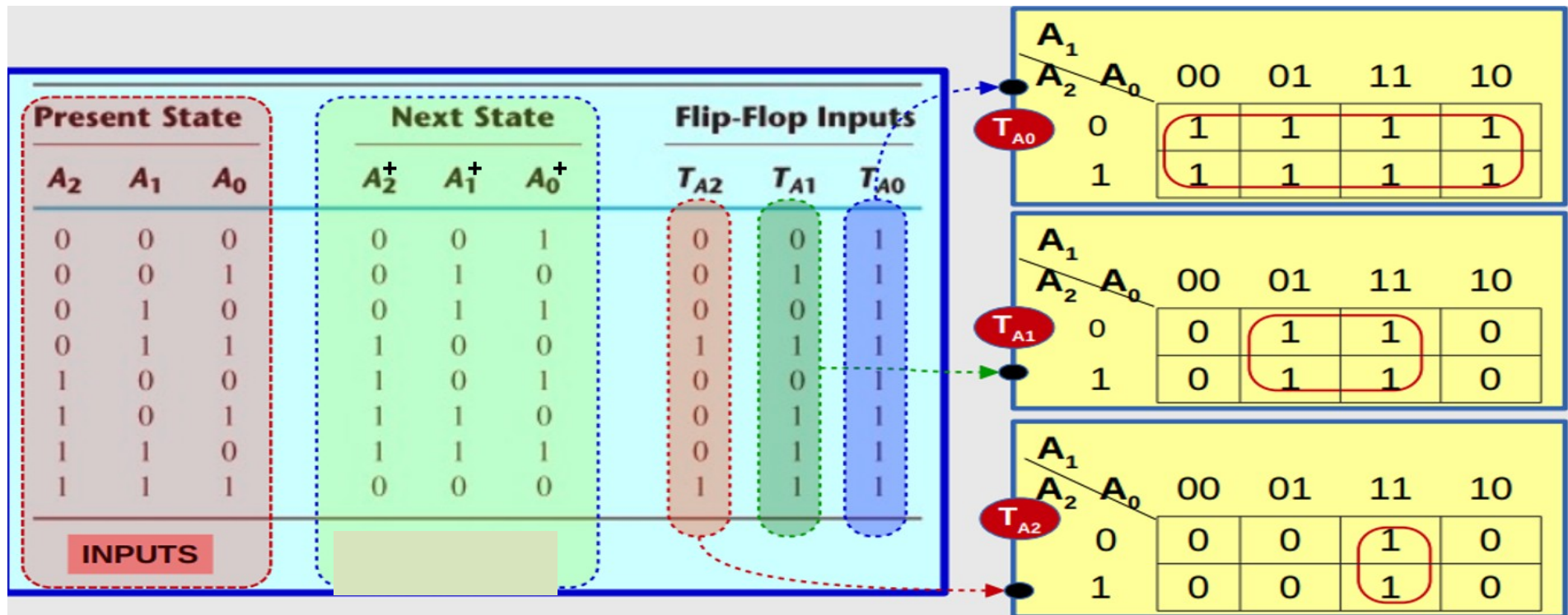

Lecture 2: Sequential Circuit


CH 1: Digital Building Blocks (Registers, Counters,.)

5- K-Map for FFs inputs and circuit Outputs

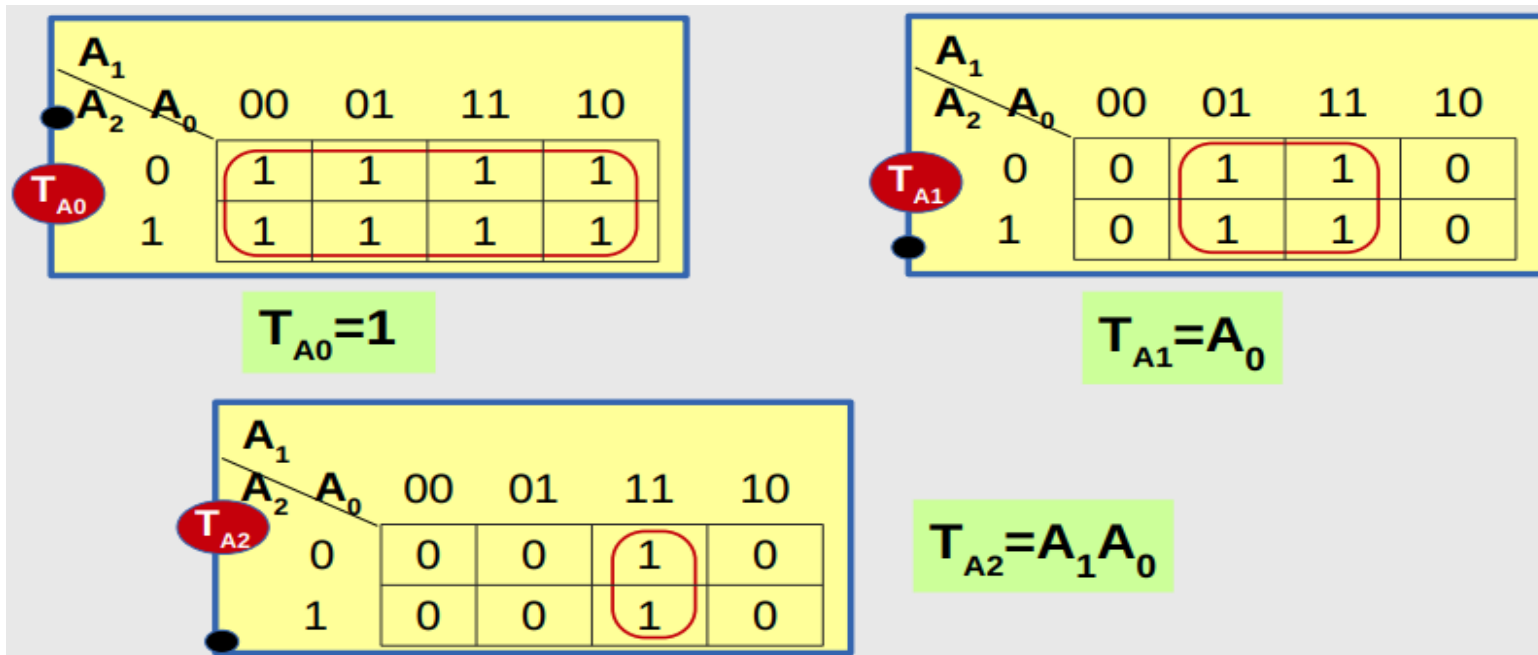

Lecture 2: Sequential Circuit

6- Circuit diagram:

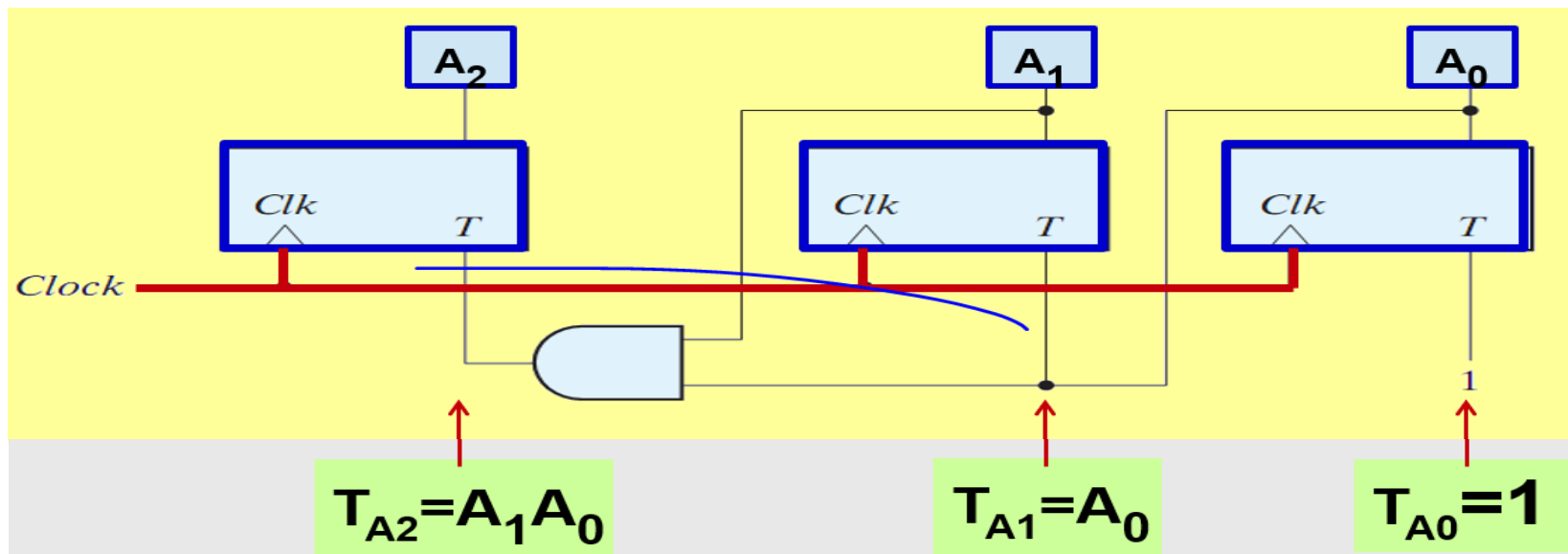


Symbol :

SYNCHRONOUS COUNTERS


SYNCHRONOUS COUNTERS

Ring Counters

 

Many digital circuits participate during a computer run to fetch and execute instructions


Symbol :

 

Controlling a sequence of operations

RING COUNTERS

 SAP-1 ring counter Hardware Implementation



Note: Pin 14 is connected to +5 V, and pin 7 is grounded.

ASYNCHRONOUS (RIPPLE) COUNTERS

RIPPLE COUNTER (Asy.)

ASYNCHRONOUS (RIPPLE) COUNTERS


-ve edge up counter (Asyn)

Count	Q_3	Q_2	Q_1	Q_0
0	0	0	0	0
1	0	0	0	1
2	0	0	1	0
3	0	0	1	1
4	0	1	0	0
5	0	1	0	1
6	0	1	1	0
7	0	1	1	1
8	1	0	0	0
9	1	0	0	1
10	1	0	1	0
11	1	0	1	1
12	1	1	0	0
13	1	1	0	1
14	1	1	1	0
15	1	1	1	1

ASYNCHRONOUS COUNTERS


ASYNCHRONOUS (RIPPLE) COUNTERS

 Controlled ripple counter(up counter –ve edge)




Symbol :

SAP-1 program counter

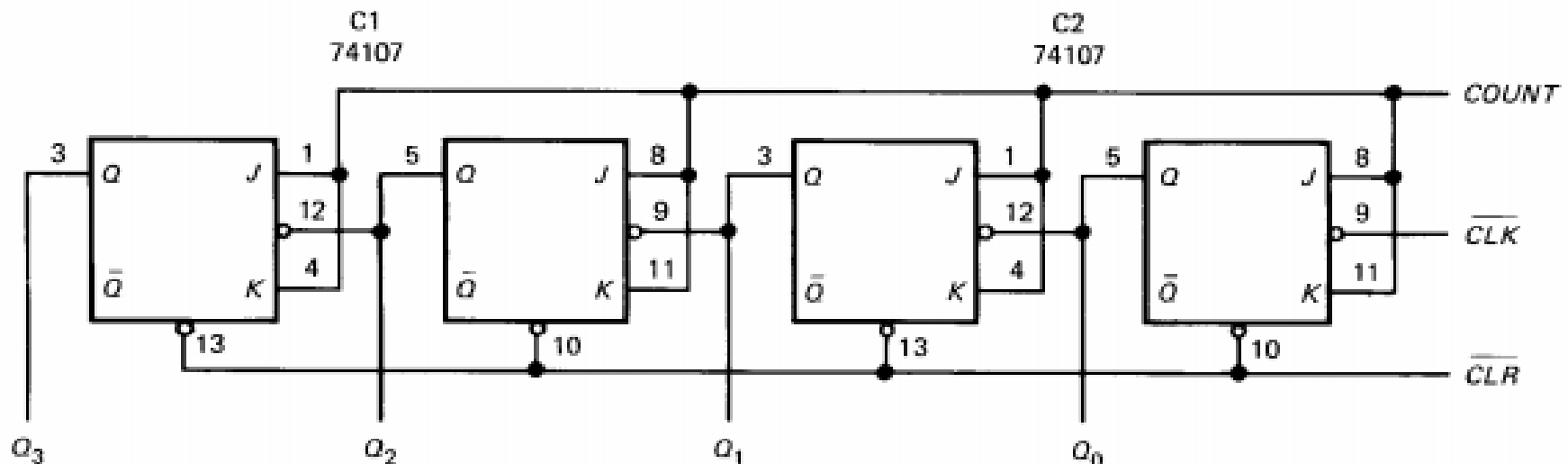

COUNTERS

Computer Components: Top-Level View

 

IAS stands for Princeton Institute for Advanced Studies. (Von Neumann)

Memory System


- **ROM**
- **RAM**

ROM Design

ROM Design

Design 8 x 4 ROM.

<i>Address</i>	<i>Data</i>
0 0 0	0 0 0 0
0 0 1	1 1 0 1
0 1 0	0 0 1 1
0 1 1	1 0 0 0
1 0 0	1 1 1 1
1 0 1	1 0 0 1
1 1 0	0 1 1 1
1 1 1	0 0 0 0

 

Types of ROMs

Mask Programmed ROM

Programmed during manufacturing

Programmable Read-Only Memory (PROM)

Blow out fuses to produce '0'

Erasable Programmable ROM (EPROM)

Erase all data by *Ultra Violet* exposure

Electrically Erasable PROM (EEPROM)

Erase the required data using an electrical signal


CH 5


MEMORY SYSTEM

Cache Memory

CH 5: MEMORY SYSTEM

The Memory Hierarchy

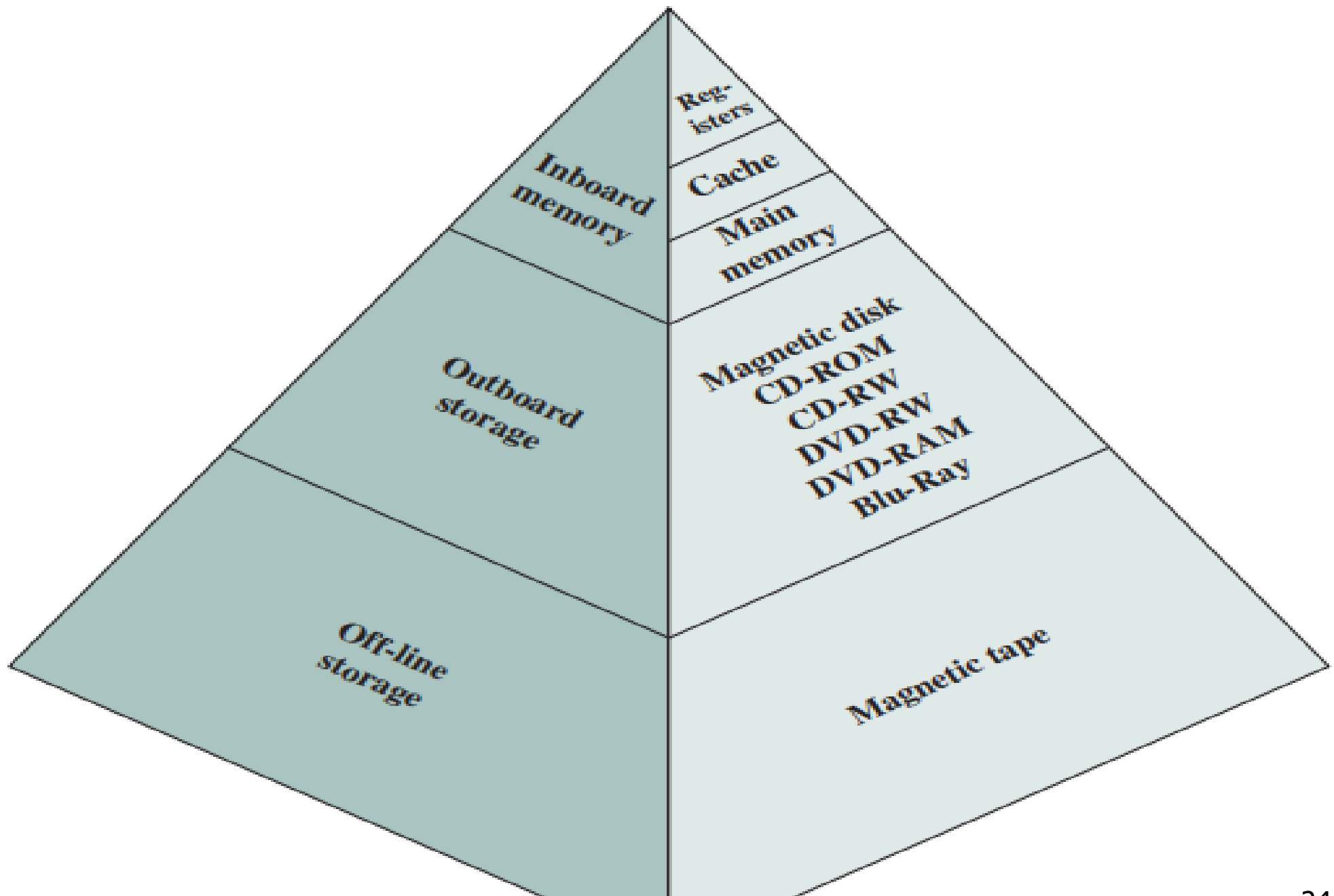

 

Questions





THANK YOU

