






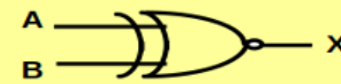


Basic Logic Gates

COMBINATIONAL GATES

Name	Symbol	Function	Truth Table															
AND		$X = A \cdot B$ or $X = AB$	<table><tr><th>A</th><th>B</th><th>X</th></tr><tr><td>0</td><td>0</td><td>0</td></tr><tr><td>0</td><td>1</td><td>0</td></tr><tr><td>1</td><td>0</td><td>0</td></tr><tr><td>1</td><td>1</td><td>1</td></tr></table>	A	B	X	0	0	0	0	1	0	1	0	0	1	1	1
A	B	X																
0	0	0																
0	1	0																
1	0	0																
1	1	1																
OR		$X = A + B$	<table><tr><th>A</th><th>B</th><th>X</th></tr><tr><td>0</td><td>0</td><td>0</td></tr><tr><td>0</td><td>1</td><td>1</td></tr><tr><td>1</td><td>0</td><td>1</td></tr><tr><td>1</td><td>1</td><td>1</td></tr></table>	A	B	X	0	0	0	0	1	1	1	0	1	1	1	1
A	B	X																
0	0	0																
0	1	1																
1	0	1																
1	1	1																
NOT		$X = A'$	<table><tr><th>A</th><th>X</th></tr><tr><td>0</td><td>1</td></tr><tr><td>1</td><td>0</td></tr></table>	A	X	0	1	1	0									
A	X																	
0	1																	
1	0																	
Buffer		$X = A$	<table><tr><th>A</th><th>X</th></tr><tr><td>0</td><td>0</td></tr><tr><td>1</td><td>1</td></tr></table>	A	X	0	0	1	1									
A	X																	
0	0																	
1	1																	
<u>NAND</u>		$X = (AB)'$	<table><tr><th>A</th><th>B</th><th>X</th></tr><tr><td>0</td><td>0</td><td>1</td></tr><tr><td>0</td><td>1</td><td>1</td></tr><tr><td>1</td><td>0</td><td>1</td></tr><tr><td>1</td><td>1</td><td>0</td></tr></table>	A	B	X	0	0	1	0	1	1	1	0	1	1	1	0
A	B	X																
0	0	1																
0	1	1																
1	0	1																
1	1	0																
NOR		$X = (A + B)'$	<table><tr><th>A</th><th>B</th><th>X</th></tr><tr><td>0</td><td>0</td><td>1</td></tr><tr><td>0</td><td>1</td><td>0</td></tr><tr><td>1</td><td>0</td><td>0</td></tr><tr><td>1</td><td>1</td><td>0</td></tr></table>	A	B	X	0	0	1	0	1	0	1	0	0	1	1	0
A	B	X																
0	0	1																
0	1	0																
1	0	0																
1	1	0																
XOR Exclusive OR		$X = A \oplus B$ or $X = A'B + AB'$	<table><tr><th>A</th><th>B</th><th>X</th></tr><tr><td>0</td><td>0</td><td>0</td></tr><tr><td>0</td><td>1</td><td>1</td></tr><tr><td>1</td><td>0</td><td>1</td></tr><tr><td>1</td><td>1</td><td>0</td></tr></table>	A	B	X	0	0	0	0	1	1	1	0	1	1	1	0
A	B	X																
0	0	0																
0	1	1																
1	0	1																
1	1	0																
<u>XNOR</u> Exclusive NOR or Equivalence		$X = (A \oplus B)'$ or $X = A'B' + AB$	<table><tr><th>A</th><th>B</th><th>X</th></tr><tr><td>0</td><td>0</td><td>1</td></tr><tr><td>0</td><td>1</td><td>0</td></tr><tr><td>1</td><td>0</td><td>0</td></tr><tr><td>1</td><td>1</td><td>1</td></tr></table>	A	B	X	0	0	1	0	1	0	1	0	0	1	1	1
A	B	X																
0	0	1																
0	1	0																
1	0	0																
1	1	1																

Rules of Boolean Algebra

$$1. A + 0 = A$$

$$2. A + 1 = 1$$

$$5. A + A = A$$

$$6. A + \bar{A} = 1$$

$$10. A + AB = A$$

$$11. A + \bar{A}B = A + B$$

$$12. (A + B)(A + C) = A + BC$$

$$3. A \cdot 0 = 0$$

$$4. A \cdot 1 = A$$

$$7. A \cdot A = A$$

$$8. A \cdot \bar{A} = 0$$

$$9. \bar{\bar{A}} = A$$

DeMorgan's Theorems



$$\overline{X + Y} = \bar{X} \bar{Y}$$

$$\overline{XY} = \bar{X} + \bar{Y}$$


Simplify using boolean Algebra

$$\begin{aligned} & AB + A(B+C) + B(B+C) \\ &= AB + AB + AC + BB + BC \\ &= AB + AC + B + BC \\ &= AB + AC + B \\ &= B + AB + AC \end{aligned}$$

$$= B + AC$$

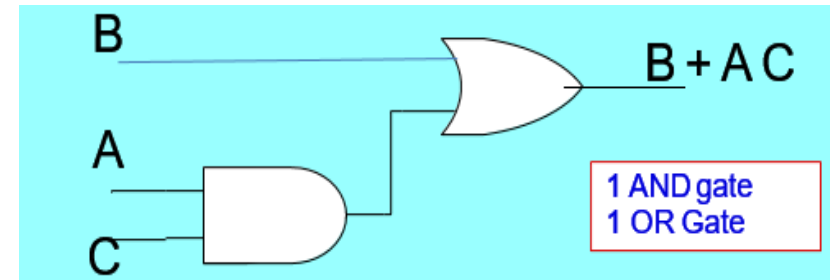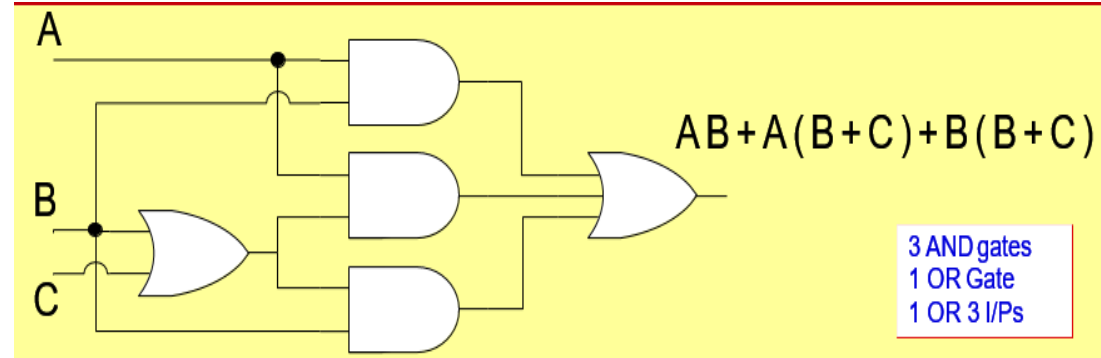

Combinational Circuit

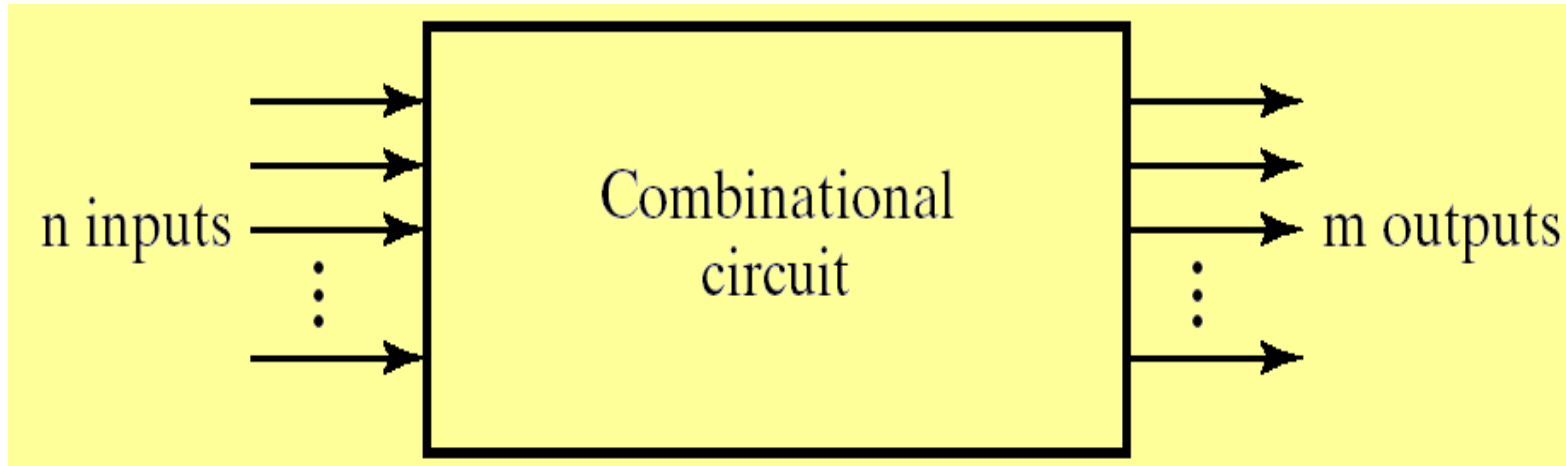


Combinational Circuits

- **Full Adder**
- **Decoder**
- **Multiplexer**

Binary Adder / Subtractor

$M=0 \rightarrow F = x + y$


$M=1 \rightarrow F = x - y$

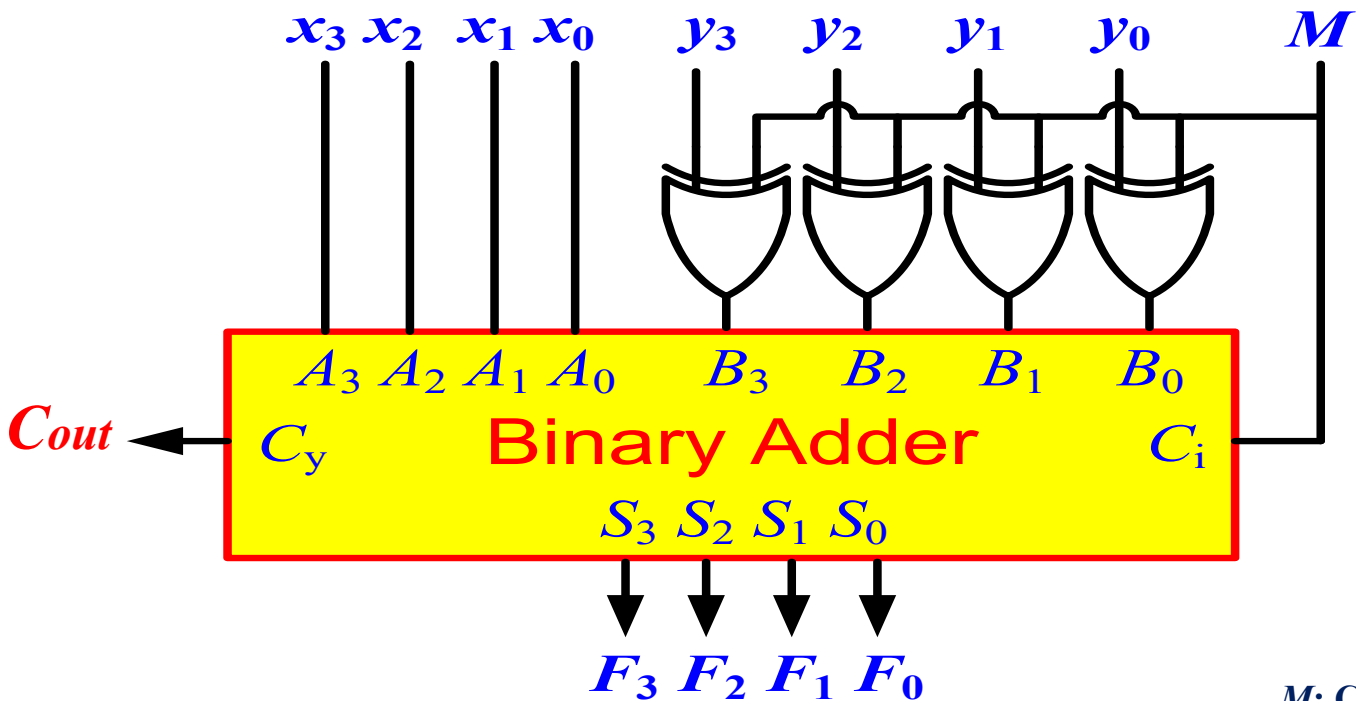

M : Control Signal Mode: Add / Sub


Carry Propagate Adder (CPA)

Adding Two 4-Bits Numbers

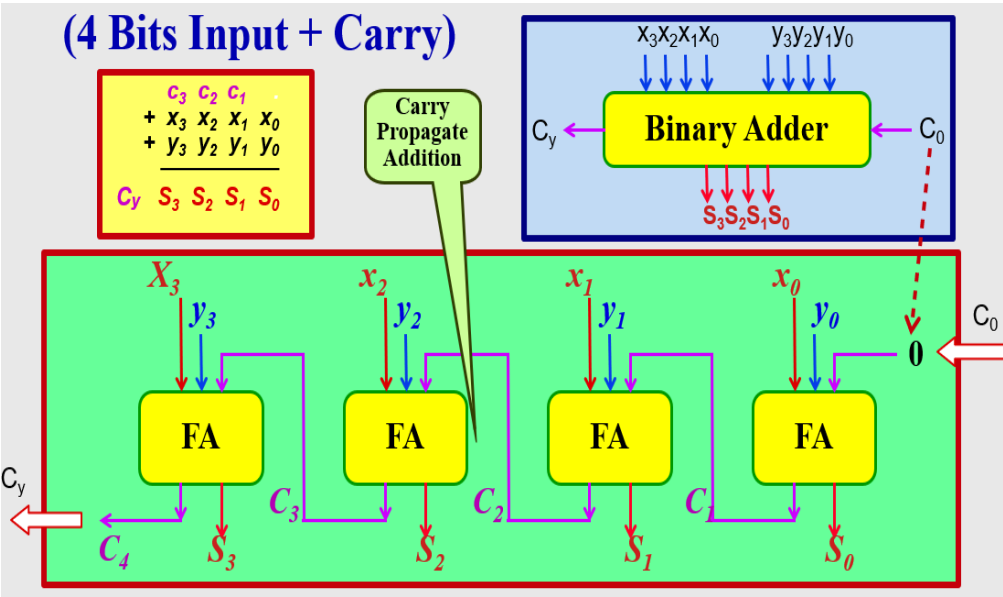

Carry Propagate Adder (CPA)


Adding Two 8-Bits Numbers

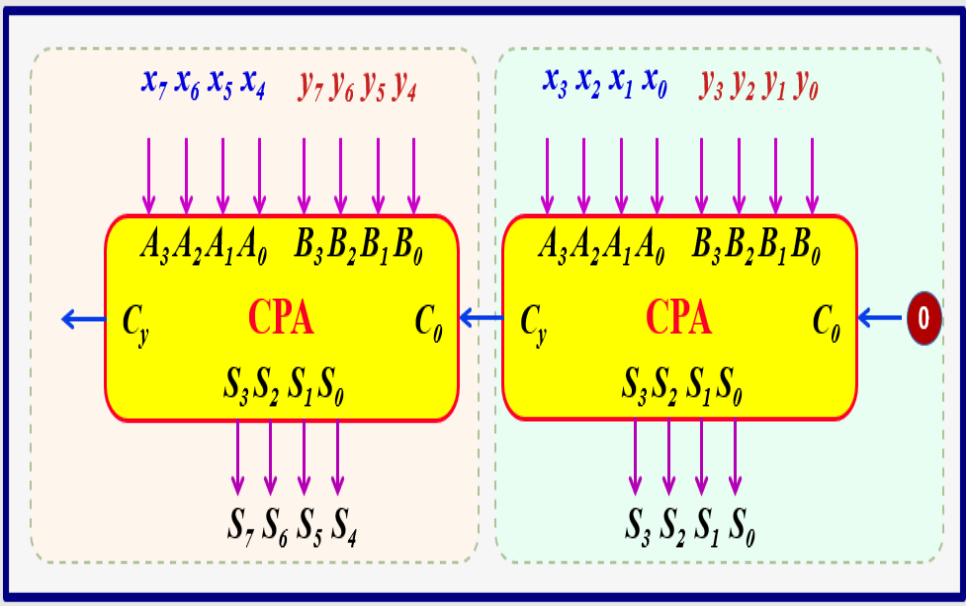



Decoders

Decoders


DEC 3x8

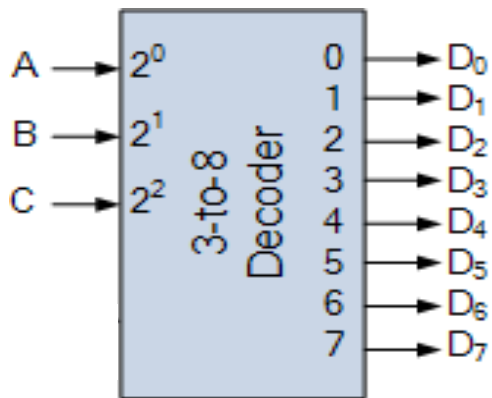

3 Input Bits

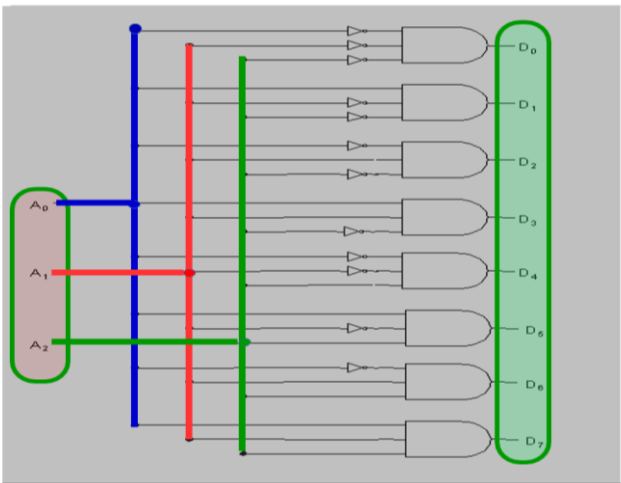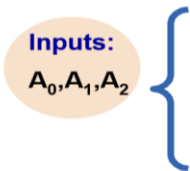

8 Output bits

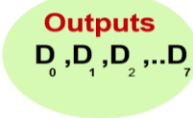


Inputs			Outputs							
A ₂	A ₁	A ₀	D ₇	D ₆	D ₅	D ₄	D ₃	D ₂	D ₁	D ₀
0	0	0	0	0	0	0	0	0	0	1
0	0	1	0	0	0	0	0	0	1	0
0	1	0	0	0	0	0	0	1	0	0
0	1	1	0	0	0	0	1	0	0	0
1	0	0	0	0	0	1	0	0	0	0
1	0	1	0	0	1	0	0	0	0	0
1	1	0	0	1	0	0	0	0	0	0
1	1	1	1	0	0	0	0	0	0	0

Decoders

DEC 2x4

2 Input Bits




A ₁	A ₀	D ₀	D ₁	D ₂	D ₃
0	0	1	0	0	0
0	1	0	1	0	0
1	0	0	0	1	0
1	1	0	0	0	1

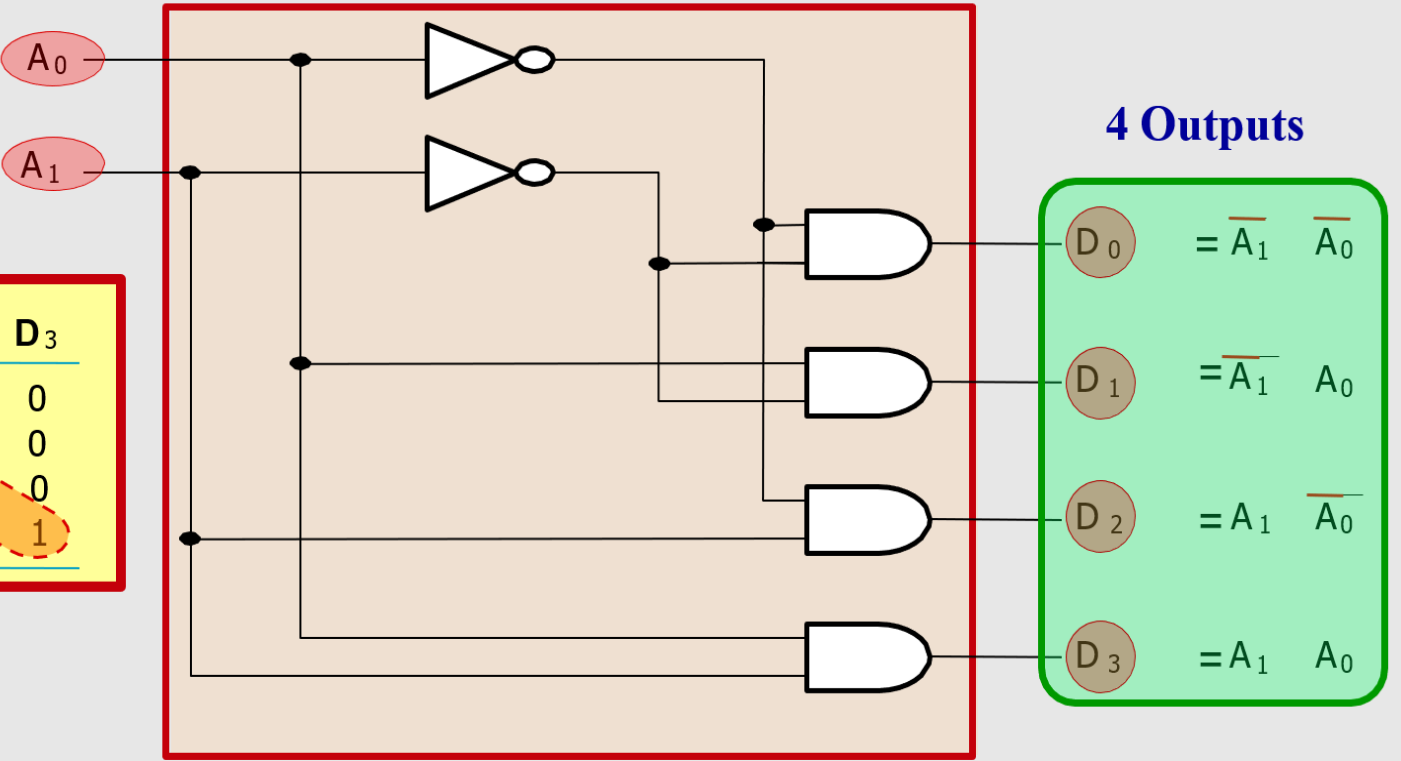


Combinational Logic Implementation using Decoder & OR Gates

Multiplexers

Multiplexers

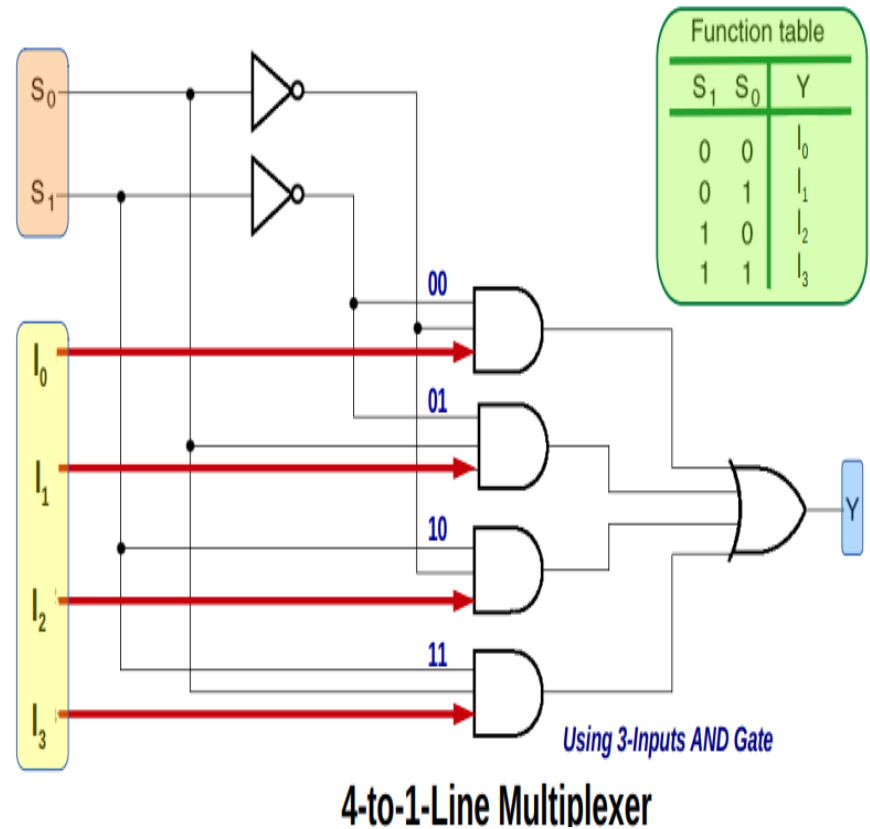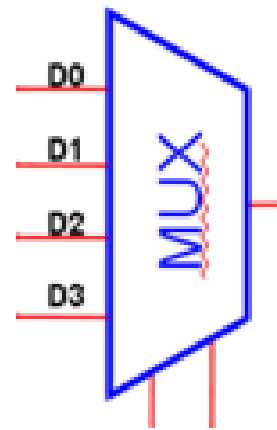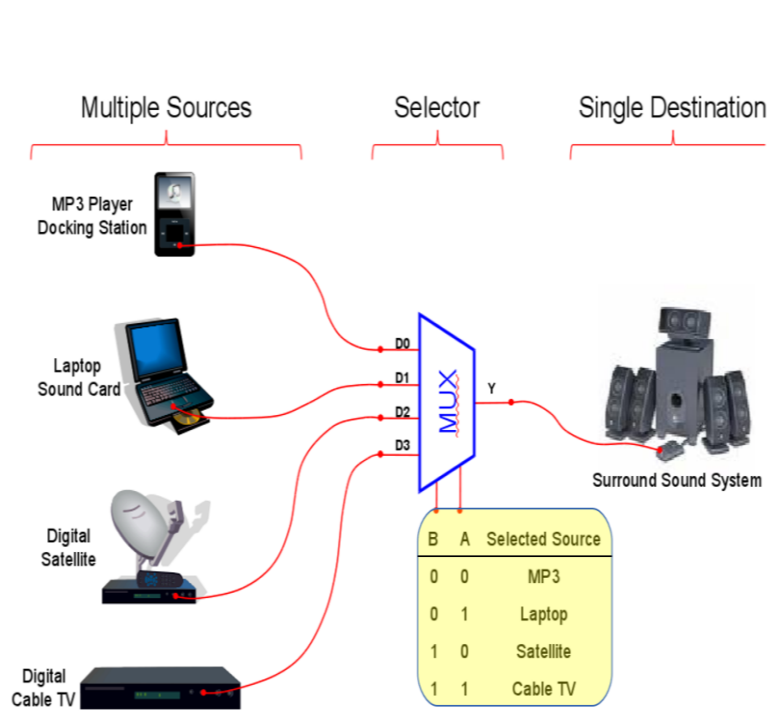

A Single Bit 4-to-1 Line Multiplexer

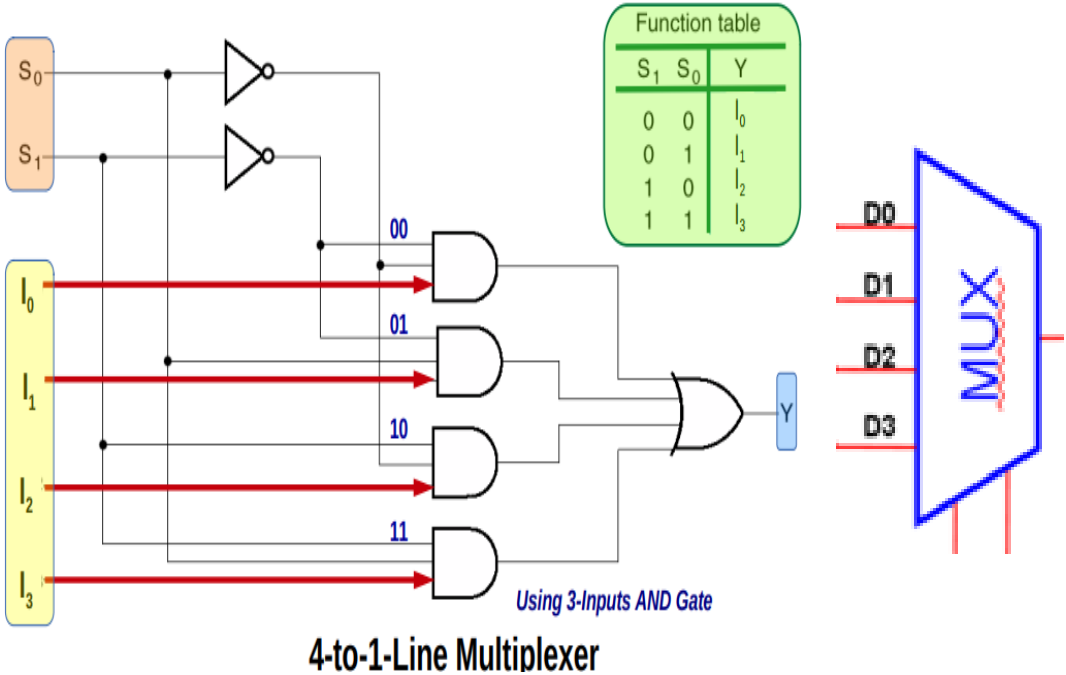

Sequential Circuits

[1] Flip Flops (FF)

[2] Design of Sequential Circuits

Review of Flip Flops

Characteristic and Excitation Table

D Flip flop

Excitation Table of “D” Flip Flop

$Q(t)$	$Q(t+1)$	D
0	0	0
0	1	1
1	0	0
1	1	1

Function Table

D	$Q(t+1)$	Output Follows Input
0	0	
1	1	

Equations

$Q(t+1) = D$

T Flip flop

Excitation Table of "T" Flip Flop

$Q(t)$	$Q(t+1)$	T
0	0	0
0	1	1
1	0	1
1	1	0

Function Table

T	$Q(t+1)$	
0	$Q(t)$	No change
1	$\bar{Q}(t)$	Toggle

$$Q(t+1) = T \oplus Q(t)$$

JK Flip flop

Simplified Excitation Table			
\Downarrow Given \Downarrow		\Uparrow Required \Uparrow	
$Q(t)$	$Q(t+1)$	J	K
$\rightarrow 0$	0	0	X
$\rightarrow 0$	1	1	X
$\rightarrow 1$	0	X	1
$\rightarrow 1$	1	X	0

Function Table			
J	K	$Q(t+1)$	
0	0	$Q(t)$	No change
0	1	0	Reset
1	0	1	Set
1	1	$\overline{Q(t)}$	Toggle

$$Q(t+1) = J\overline{Q(t)} + \overline{K}Q(t)$$


Design of Sequential Circuit

Example:


Design a 3 bit Counter (Using “T” FF) which counts in binary form as follows;
000, 001, 010, ... 111, 000, 001, ...

Solution


2- State diagram:

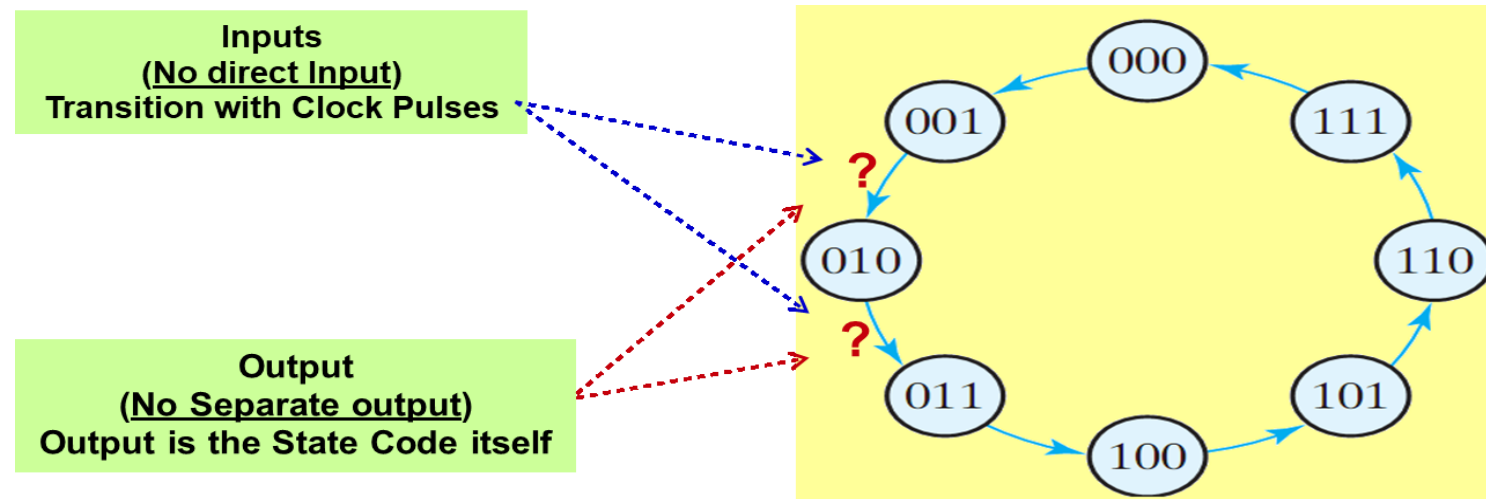


4- State Table:

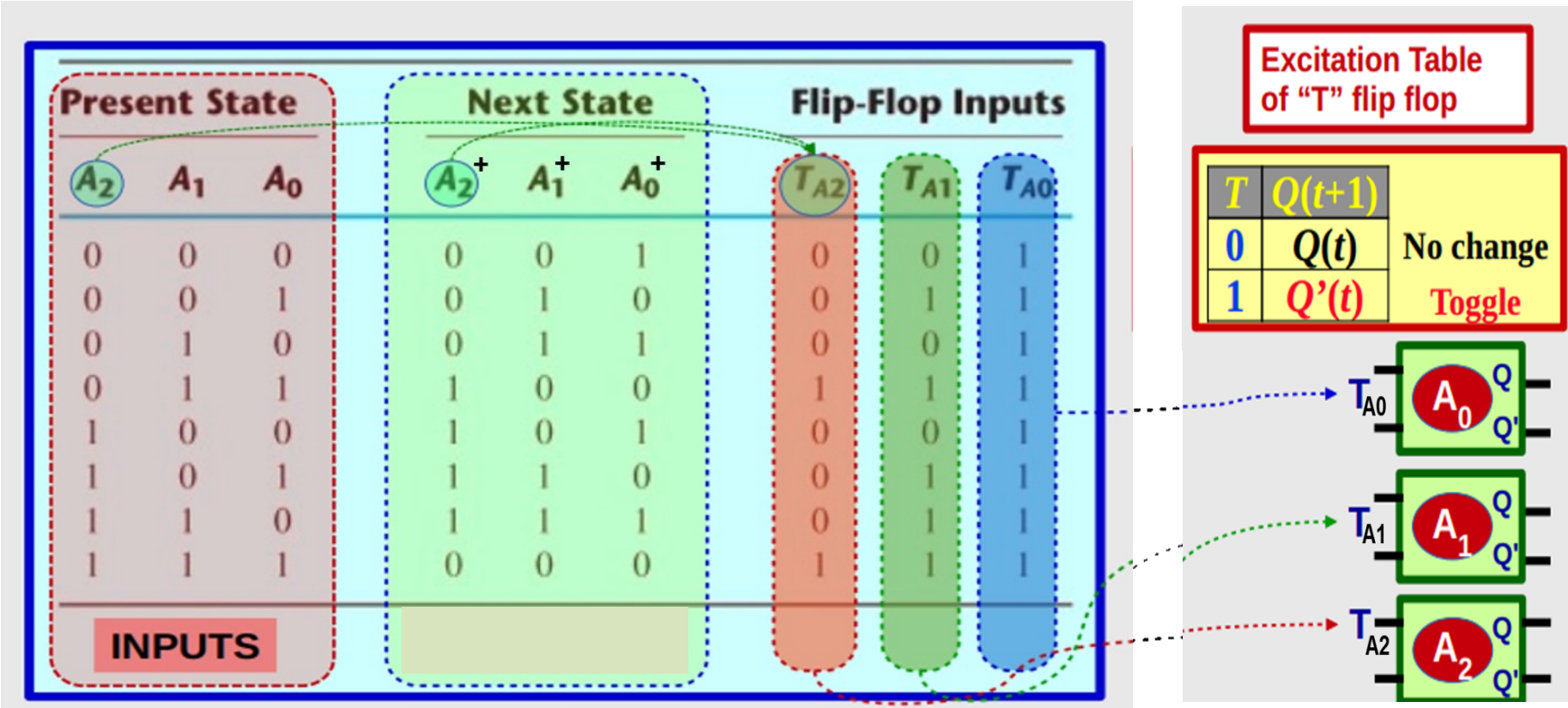

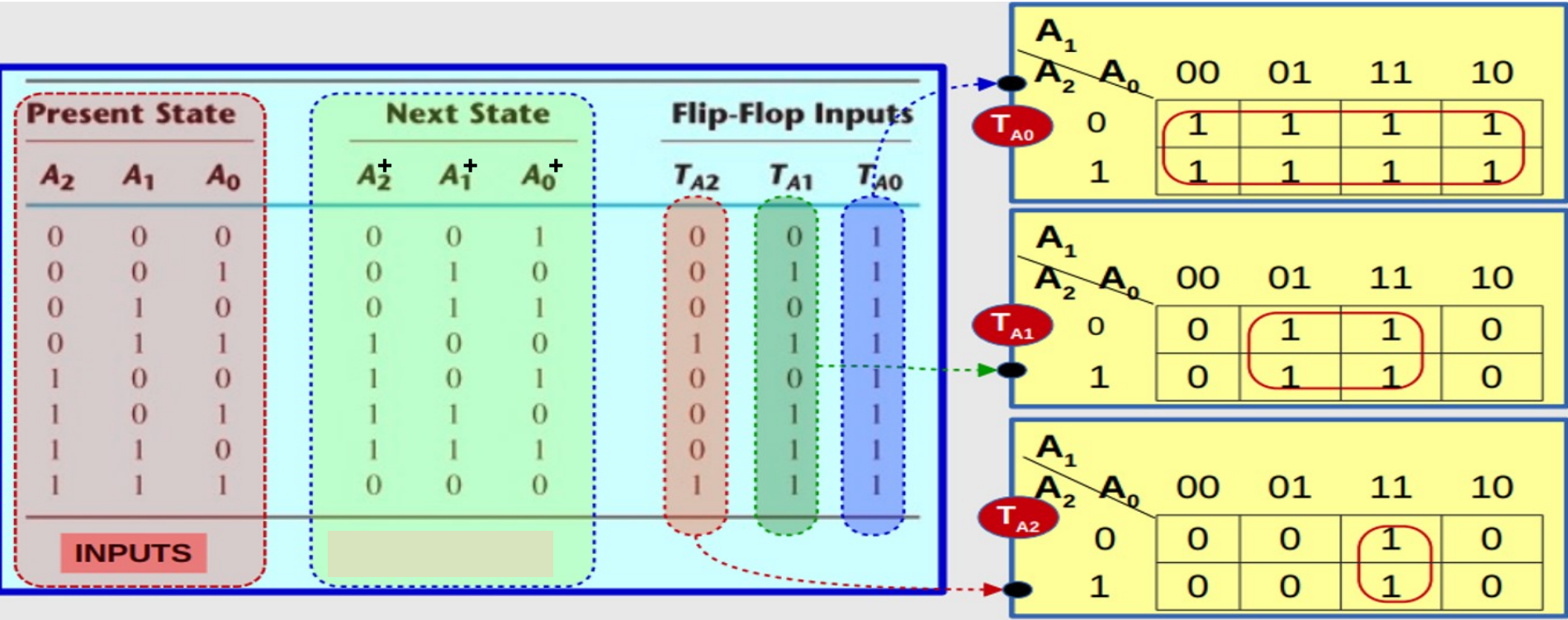5- K-Map for FFs inputs and circuit Outputs



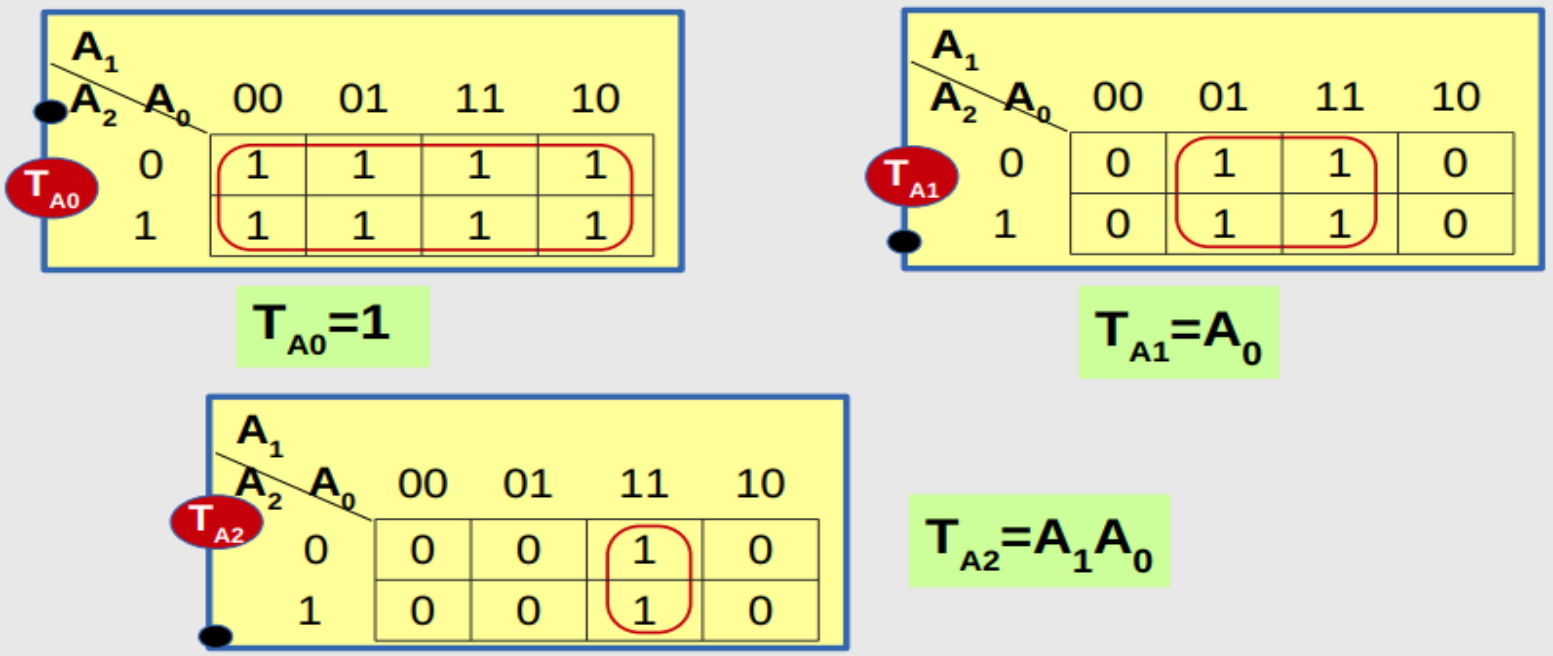5- K-Map for FFs inputs and circuit Outputs



6- Circuit diagram:

